
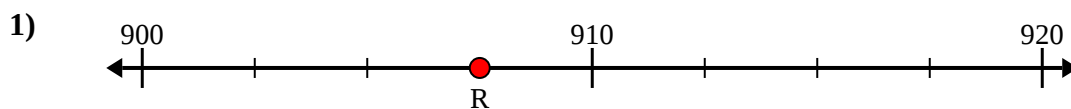


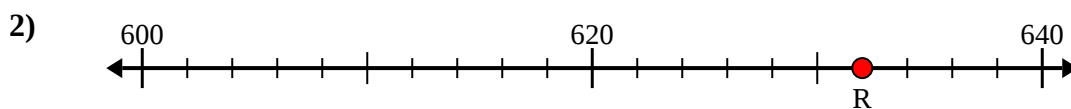


Finde den Wert von R.

Antworten


1. _____




2. _____

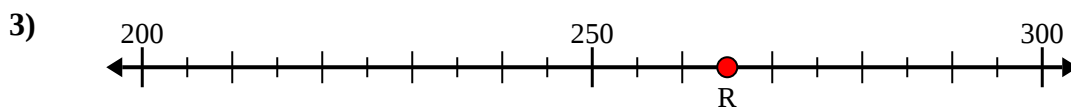


3. _____

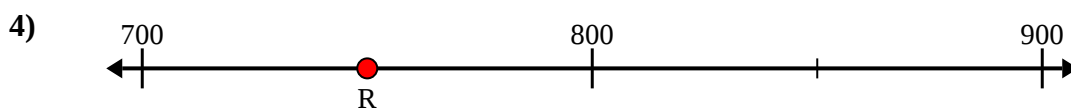


4. _____

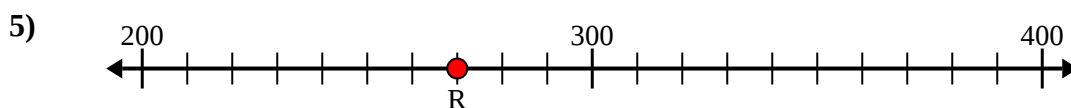


5. _____

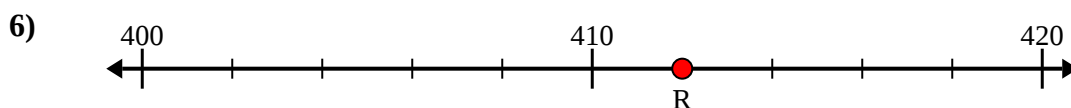


6. _____

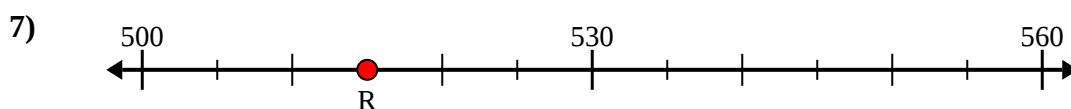


7. _____

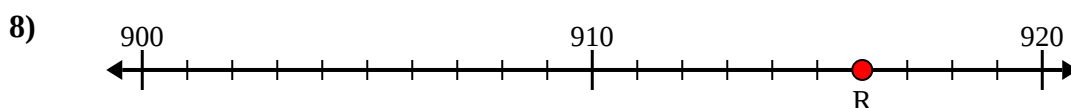

8. _____

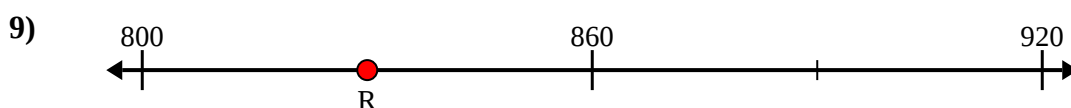











9. _____

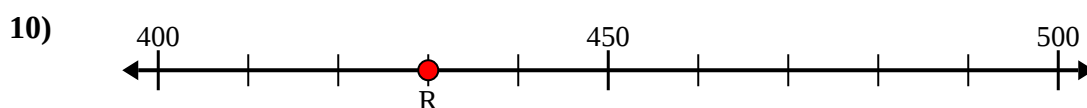

10. _____



Finde den Wert von R.

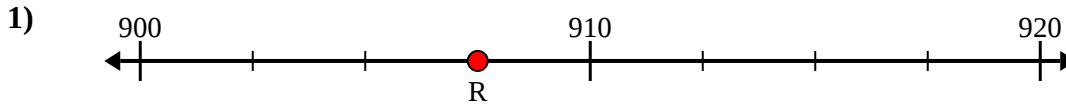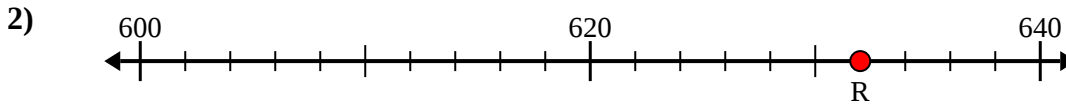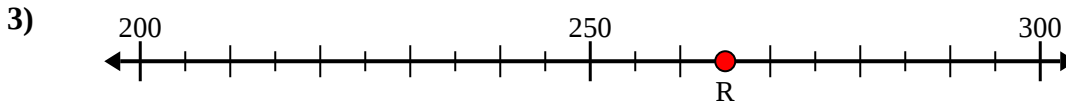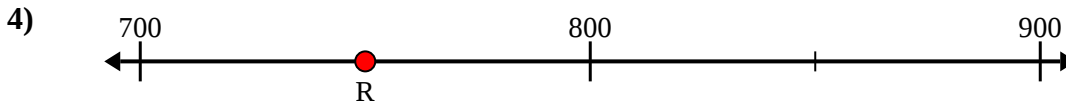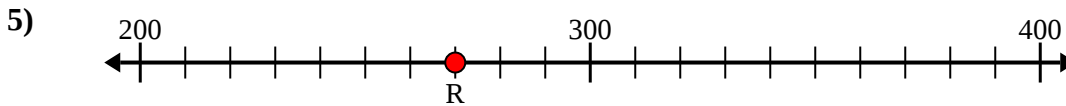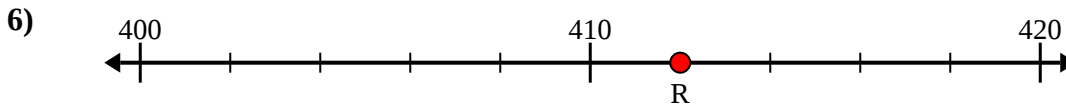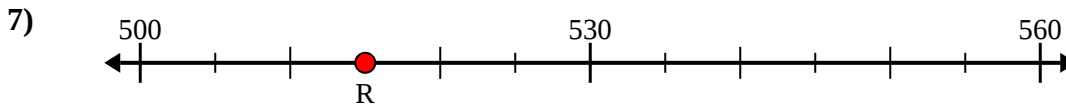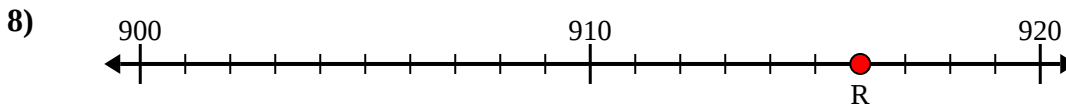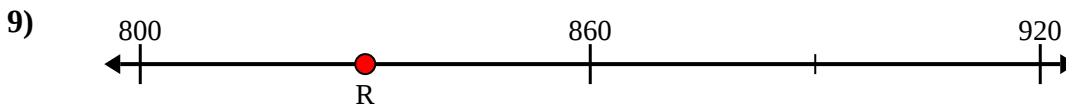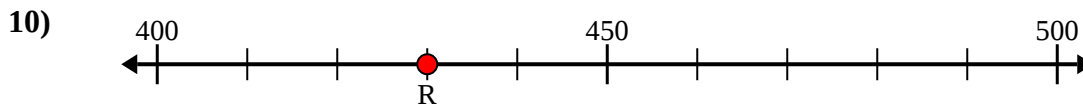Antworten1. **907,5**2. **632**3. **265**4. **750**5. **270**6. **412**7. **515**8. **916**9. **830**10. **430**