
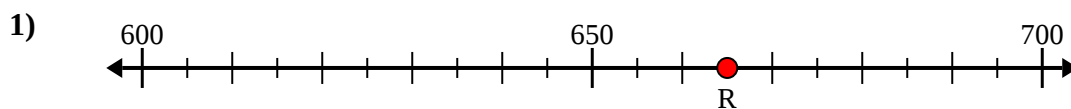


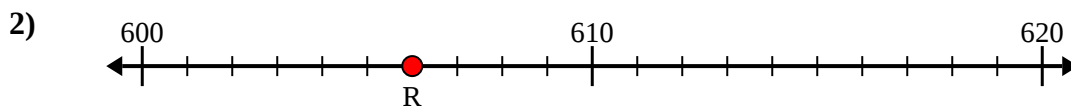


Finde den Wert von R.

Antworten


1. _____




2. _____

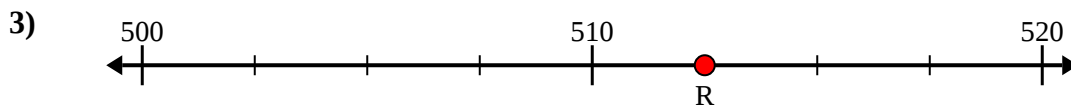


3. _____

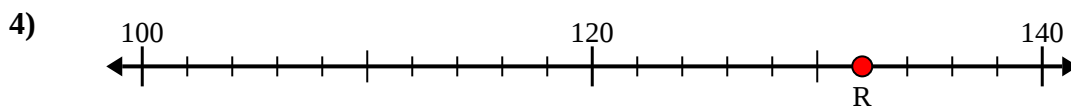


4. _____

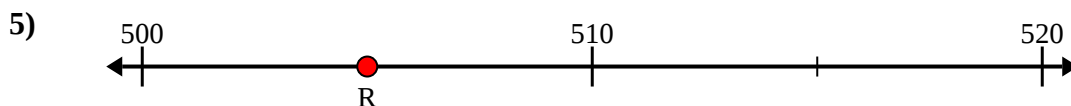


5. _____

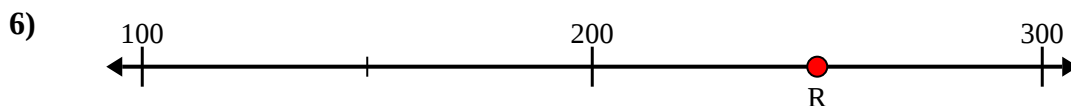


6. _____

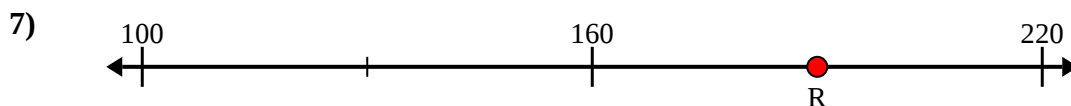


7. _____

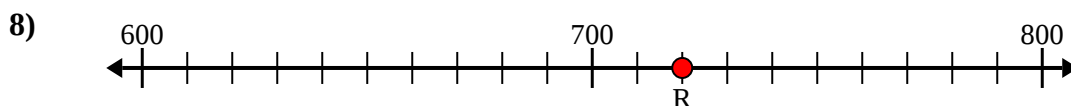

8. _____

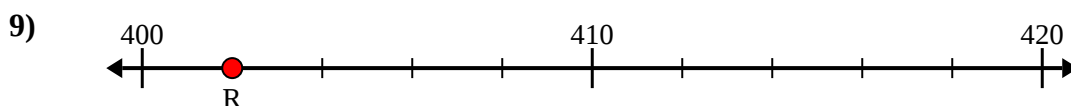











9. _____

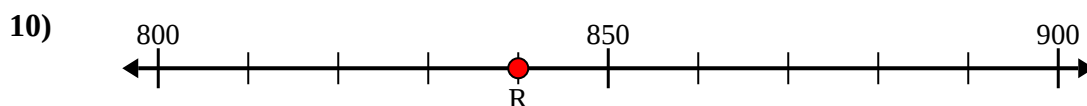

10. _____



Finde den Wert von R.

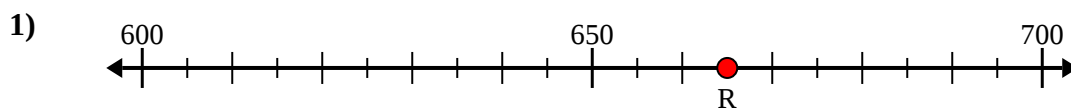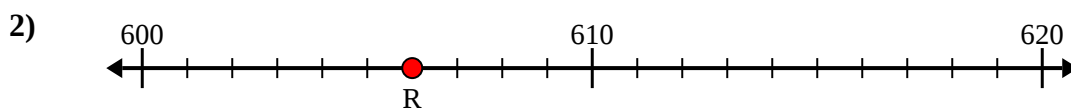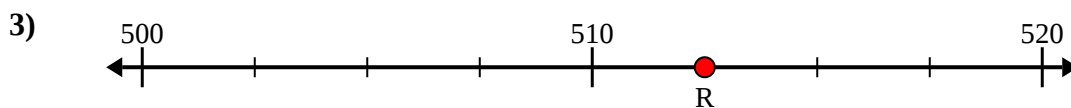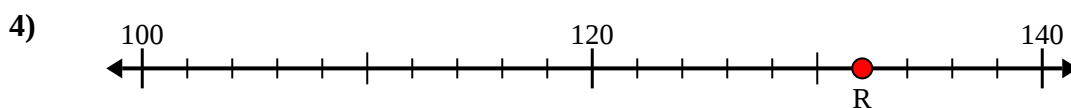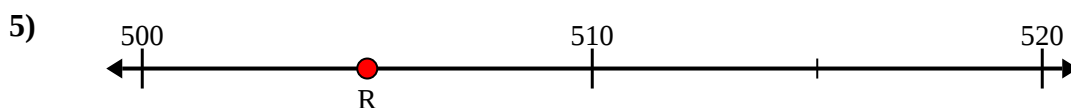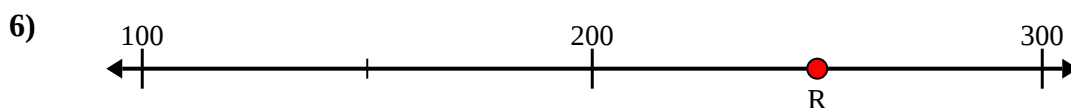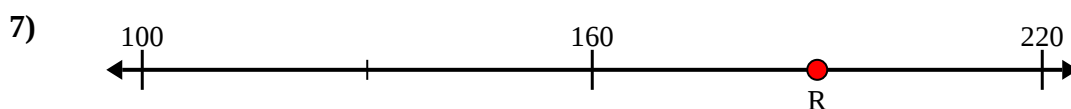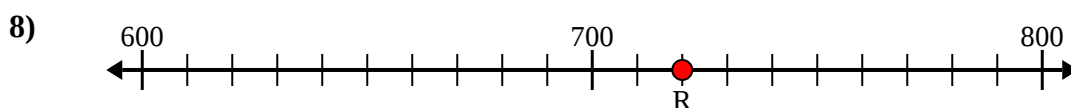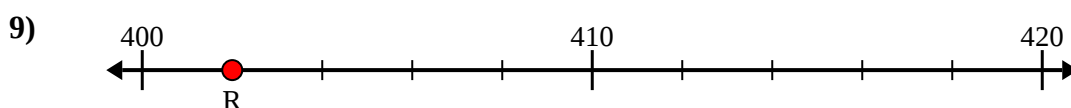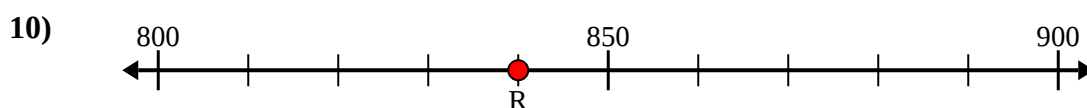Antworten1. 6652. 6063. 512,54. 1325. 5056. 2507. 1908. 7209. 40210. 840