
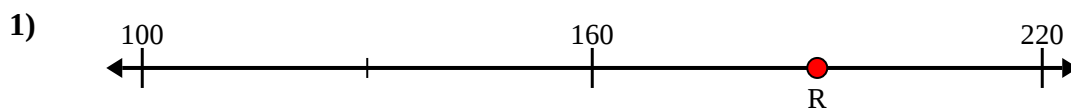


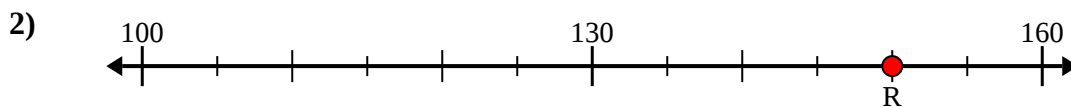


Finde den Wert von R.

Antworten


1. _____




2. _____

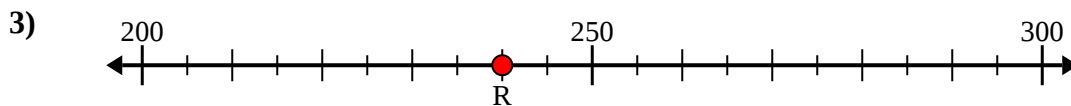


3. _____

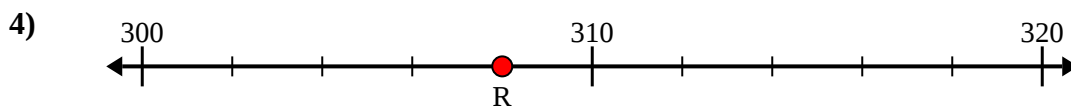


4. _____

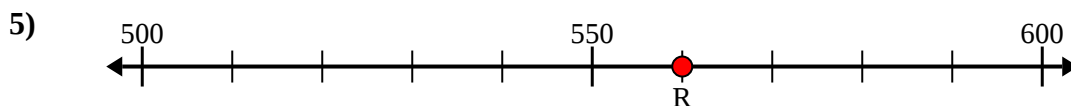


5. _____

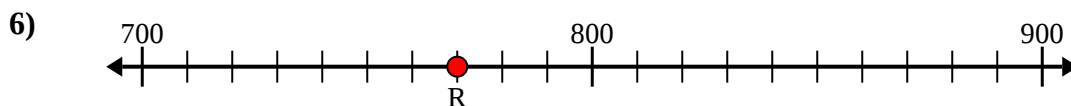


6. _____

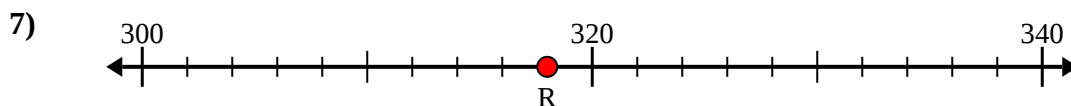


7. _____

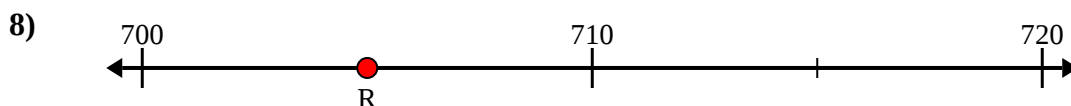

8. _____

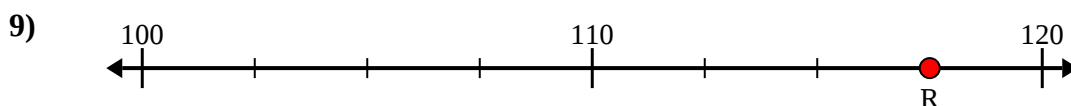











9. _____

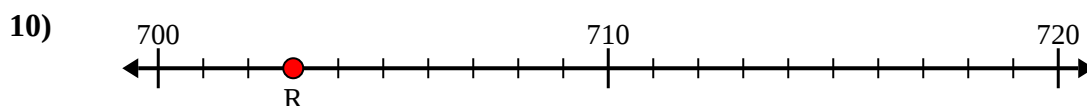

10. _____



Finde den Wert von R.

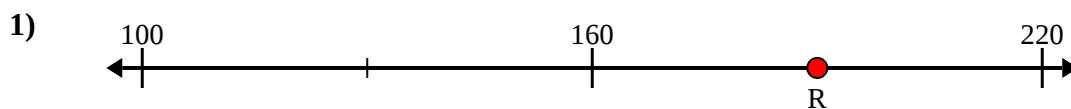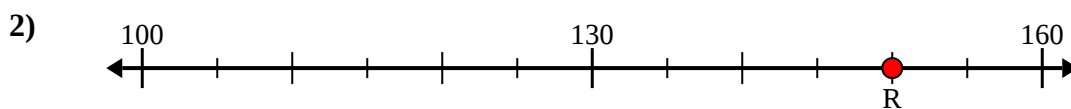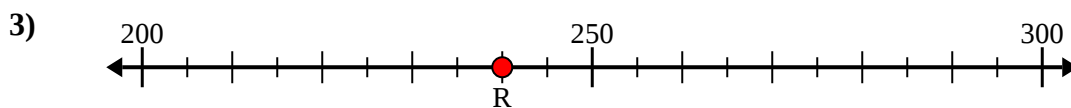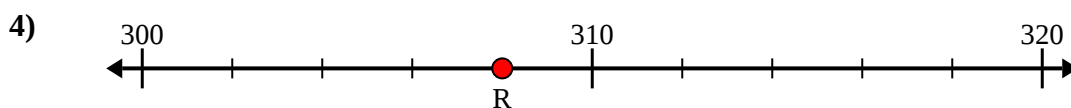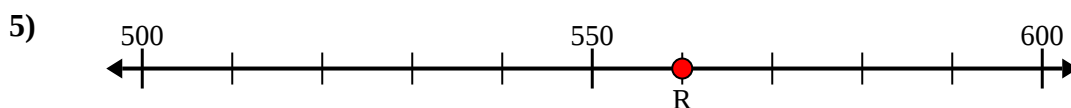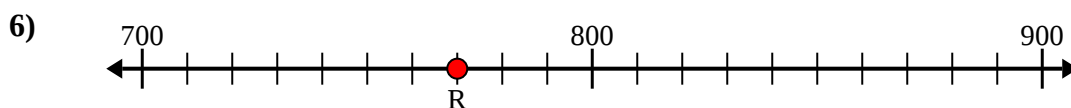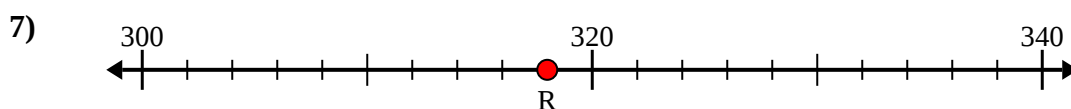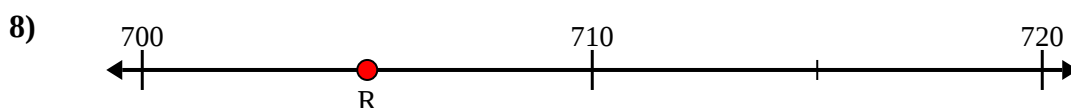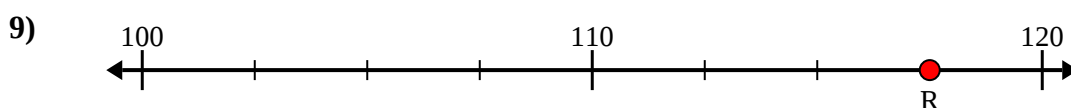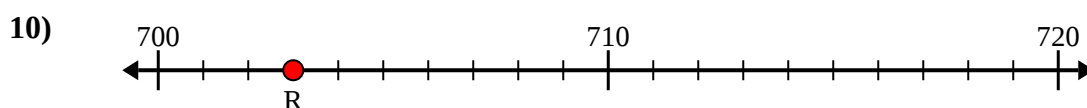Antworten1. **190**2. **150**3. **240**4. **308**5. **560**6. **770**7. **318**8. **705**9. **117,5**10. **703**